

Power Electronics Education Electronic Book



Welcome to PEEEB






Tutorial 3: Diode Rectifiers

Presenter: Dr. Firuz Zare

www.peeeb.com

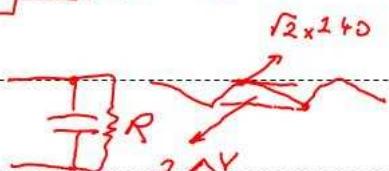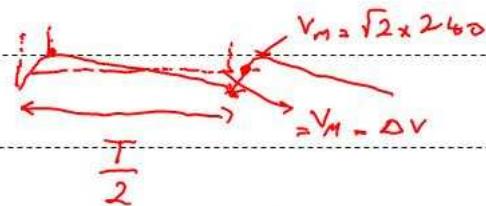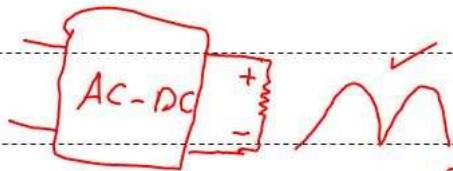Q1: A single-phase diode rectifier with R-C load is connected to a grid with 240 V and 50 Hz. Find C value to have 20V ripple on the output side when output power is 100 watts.

$$V_{in} = \sqrt{2} \times 240 \times \sin\left(\frac{2\pi t}{T}\right)$$



$$\frac{V_{out}}{R} = i_R = \frac{V_m - \Delta V}{R}$$

$$C \frac{dV_c}{dt} = i_C \Rightarrow C \times \frac{-2\Delta V}{\frac{T}{2}} = -i_R$$

$$-C \times \frac{4\Delta V}{T} = -\left(\frac{V_m - \Delta V}{R}\right)$$



Presenter: Dr. Firuz Zare

www.peeeb.com

$$4 Cf \Delta V = \frac{V_m - \Delta V}{R}$$

$$I \times R \cdot \frac{V_{out}}{I} = \frac{V_{out}^2}{P_{out}}$$

$$4 Cf R \Delta V = V_m - \Delta V$$


$$f = 50 \text{ Hz}$$

$$\Delta V = 20 \text{ V}$$

$$\Delta V (1 + 4 R C f) = V_m$$


$$\Delta V = \frac{V_m}{1 + 4 R C f} \rightarrow V_m = \sqrt{2} \times 240$$

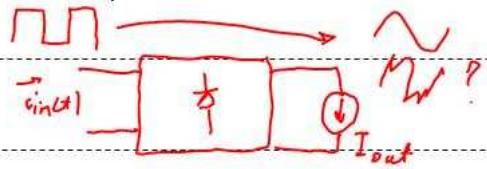Q2: A single-phase diode rectifier is connected to a pure inductive load in which the load current, I_{out} is constant. Find the input current and its harmonics.



$$i_{in(t)} = \frac{a_0}{2} + \sum a_n \cos\left(\frac{2\pi t}{T} \times n\right) + b_n \sin\left(\frac{2\pi t}{T} \times n\right)$$
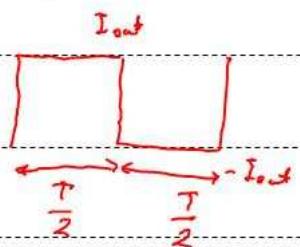
$$a_0 = \frac{2}{T} \int_0^T i_{in(t)} dt \Rightarrow a_0 = 0$$



$$a_n = \frac{2}{T} \int_0^T i_{in(t)} \cos\left(\frac{2\pi t}{T} \times n\right) dt$$

$$b_n = \frac{2}{T} \int_0^T i_{in(t)} \sin\left(\frac{2\pi t}{T} \times n\right) dt$$

$$\begin{aligned}
 a_n &= \frac{2}{T} \int_0^{\frac{T}{2}} I_{\text{out}} * \cos\left(\frac{2\pi t}{T} \times n\right) dt + \frac{2}{T} \int_{\frac{T}{2}}^T (-I_{\text{out}}) * \cos\left(\frac{2\pi t}{T} \times n\right) dt \\
 &= \cancel{\frac{2}{T} I_{\text{out}} \times \left(\frac{T}{2\pi n}\right)} \overset{0}{\cancel{\sum}} \left(\frac{2\pi t}{T} \times n \right) \Big|_0^{\frac{T}{2}} + \cancel{\frac{2}{T} (-I_{\text{out}}) \times \left(\frac{T}{2\pi n}\right)} \overset{0}{\cancel{\sum}} \left(\frac{2\pi t}{T} \times n \right) \Big|_{\frac{T}{2}}^T \\
 \sin\left(\frac{2\pi T}{T} \times n\right) &= \sin(\pi n) = 0 \\
 \sin(0) &= 0
 \end{aligned}$$

$$a_n = 0$$

$$b_n = ?$$

$$\begin{aligned}
 b_n &= \frac{2}{T} \int_0^{\frac{T}{2}} I_{\text{out}} * \sin\left(\frac{2\pi t}{T} + n\right) dt + \frac{2}{T} \int_{\frac{T}{2}}^T (-I_{\text{out}}) * \sin\left(\frac{2\pi t}{T} + n\right) dt \\
 &= \frac{2 I_{\text{out}}}{T} \times \left(-\frac{T}{2\pi n} \right) \left[\cos\left(\frac{2\pi t}{T} + n\right) \right]_0^{\frac{T}{2}} + \frac{2 \times (-I_{\text{out}})}{T} \times \left(-\frac{T}{2\pi n} \right) \times \left[\cos\left(\frac{2\pi t}{T} + n\right) \right]_{\frac{T}{2}}^T \\
 &= -\frac{4 I_{\text{out}}}{2\pi n} \left[\cos\left(\frac{2\pi T}{2\pi} + n\right) - \cos(n) \right] + \frac{2 I_{\text{out}}}{2\pi n} \left[\cos\left(\frac{2\pi T}{T} + n\right) - \cos\left(\frac{2\pi T}{2\pi} + n\right) \right] \\
 &\approx -\frac{I_{\text{out}}}{\pi n} \left[\cos(n+1) - 1 \right] + \frac{I_{\text{out}}}{\pi n} \left[\cos(2\pi n) - \cos(n) \right] \\
 n &= 2, 4, 6, \dots \\
 n &= 1, 3, 5, \dots \quad \frac{2 I_{\text{out}}}{\pi n} + \frac{2 I_{\text{out}}}{\pi n} = \frac{4 I_{\text{out}}}{\pi n} \quad b_1 = \frac{4 I_{\text{out}}}{\pi} \\
 b_3 &= \frac{4 I_{\text{out}}}{\pi^3}
 \end{aligned}$$

Presenter: Dr. Firuz Zare

www.peeeb.com