



Welcome to PEEEB



*Tutorial 6: Non-isolated DC-DC Converters
with Real Components*

Presenter: Dr. Firuz Zare

www.peeeb.com

Q1: In a boost converter with $V_{in}=5$ V, $R= 10$ Ohms, $R_L=0.01$ Ohms and $V_D=0.8$ V, what are output voltages for $D=[0.1, 0.5, 0.9]$ when the converter operates in CCM?

$$\frac{V_{out}}{V_{in}} = \frac{1}{D'K_{Boost}} - \frac{DV_S}{D'K_{Boost}V_{in}} - \frac{V_D}{K_{Boost}V_{in}} \quad K_{Boost} = \left(1 + \left[\frac{R_{in} + R_L + (DR_S + DR_D)}{D'^2 R} \right] \right)$$

$$V_{out} = \left(\frac{V_{in}}{D'} - V_D \right) \times \frac{1}{K_{Boost}}$$

$$K_{Boost} = \left(1 + \frac{R_L}{D'^2 \times R} \right)$$

$$D = 0.1 \Rightarrow D' = 0.9$$

$$V_{out} = \left(\frac{5}{0.9} - 0.8 \right) \times \frac{1}{\left(1 + \frac{0.01}{(0.9)^2 \times 10} \right)} = 4.75$$

↙ 1.001
↘ 5.55

$$D = 0.5 \Rightarrow D' = 0.5$$

$$= \left(\frac{5}{0.5} - 0.8 \right) \times \frac{1}{\left(1 + \frac{0.01}{(0.5)^2 \times 10} \right)} = 9.16 \text{ V}$$

↘ 10 V

$$D = 0.9 \Rightarrow D' = 0.1$$

$$= \left(\frac{5}{0.1} - 0.8 \right) \times \frac{1}{\left(1 + \frac{0.01}{(0.1)^2 \times 10} \right)} = 44.72$$

↙ 1.1
→ 50

Presenter: Dr. Firuz Zare

www.peeeb.com

Q2: What are duty cycles for a buck-boost converter to generate $V_{out}=24V$ when $12 < V_{in} < 48$. The converter operates in CCM and $V_S=2.4V$, $V_D=0.8V$.

$$\frac{V_{out}}{V_{in}} = \frac{D}{D'K_{Buck-Boost}} = \frac{DV_S}{D'K_{Buck-Boost}V_{in}} = \frac{V_D}{K_{Buck-Boost}V_{in}}$$

$$K_{Buck-Boost} = 1 + \frac{1}{D'^2 R} (D(R_{in} + R_S + R_L) + D'(R_D + R_L))$$

≈ 1

$$V_{out} = V_{in} \times \frac{D}{D'} = \frac{D}{D'} \times V_S = V_D$$

Presenter: Dr. Firuz Zare

www.peeeb.com

$$24 = \frac{D}{1-D} \times 12 - \frac{D}{1-D} \times 2.4 - 0.8$$

$$24.8 = \frac{D}{1-D} \times 9.6 \Rightarrow \boxed{D \approx 0.72}$$
$$0.352 < D < 0.72$$

$$24 = \frac{D}{1-D} \times 48 - \frac{D}{1-D} \times 2.4 - 0.8$$

$$24.8 = \frac{D}{1-D} \times 45.6 \Rightarrow \boxed{D = 0.352}$$

Presenter: Dr. Firuz Zare

www.peeeb.com