



Welcome to PEEEB



Tutorial 4: Controlled Rectifiers

Presenter: Dr. Firuz Zare

www.peeeb.com

Q1: A single-phase full-wave controlled rectifier with a pure resistive load is connected to a power supply of 240V and 50 Hz.

(a) What are firing angles to obtain 100 V and 50 V?

(b) Compare the results with an inductive load (continuous current) ?


$$V_{out} = \frac{V_m}{\pi} [1 + \cos(\alpha)]$$

$$100 = \frac{\sqrt{2} \times 240}{\pi \rightarrow 3.14} [1 + \cos(\alpha)]$$


$$\frac{314}{\sqrt{2} \times 240} = 1 + \cos(\alpha)$$

$$\cos(\alpha) = \frac{314}{\sqrt{2} \times 240} - 1 \rightarrow \alpha = 94^\circ$$
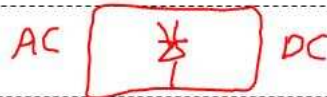
$$\cos(\alpha) = \frac{50 \times 3.14}{\sqrt{2} \times 240} - 1 \rightarrow \alpha = 122^\circ$$



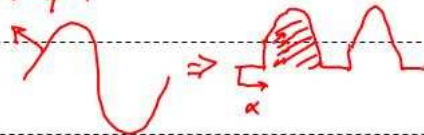
$$V_m \sin\left(\frac{2\pi t}{T}\right)$$



Presenter: Dr. Firuz Zare

www.peeeb.com
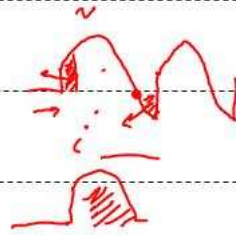
$$V_{out} = \frac{2V_m}{\pi} \cos(\alpha)$$




$$100 = \frac{2 \times \sqrt{2} \times 240}{3.14} \times \cos(\alpha)$$

	(L)	R
$\cos(\alpha) = \frac{314}{\sqrt{2} \times 480} \Rightarrow \alpha = 6.2^\circ$	}	$\alpha = 94^\circ$
$\cos(\alpha) = \frac{50 \times 3.14}{\sqrt{2} \times 480} \Rightarrow \alpha = 78^\circ$	}	$\alpha = 122^\circ$

Presenter: Dr. Firuz Zare

www.pceeb.com

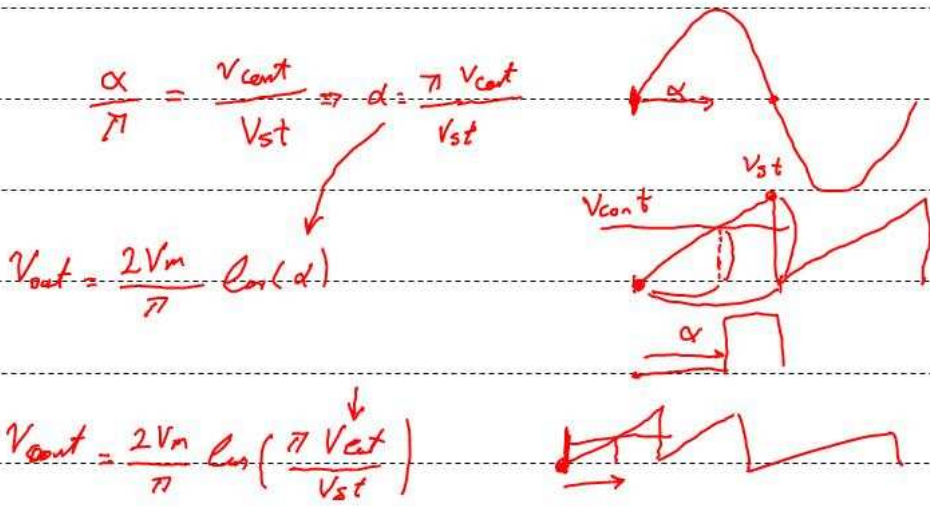
Q2: Compare a linear and a nonlinear firing angle control circuits for a controlled rectifier.



Presenter: Dr. Firuz Zare


www.pceeb.com
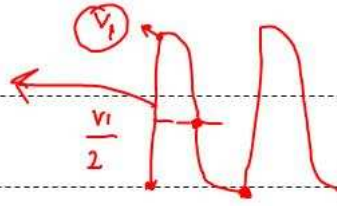
$$f(t) = \frac{V_1 \left[\cos\left(\frac{2\pi t}{T}\right) + 1 \right]}{2}$$



$$f(0) = \frac{V_1 \left[\cos(0) + 1 \right]}{2} = \frac{V_1 \times 2}{2} = V_1$$
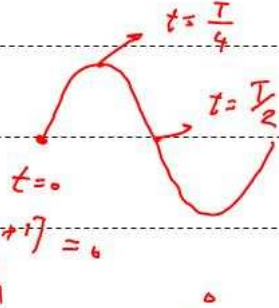
$$f\left(\frac{T}{2}\right) = \frac{V_1 \left[\cos\left(\frac{2\pi T}{2T}\right) + 1 \right]}{2} = \frac{V_1}{2} \left[\cos(\pi) + 1 \right] = 0$$



$$f\left(\frac{T}{4}\right) = \frac{V_1 \left[\cos\left(\frac{2\pi}{T} \times \frac{T}{4}\right) + 1 \right]}{2} = \frac{V_1 \left[\cos\left(\frac{\pi}{2}\right) + 1 \right]}{2} = \frac{V_1}{2}$$

$$\overline{V_{out}} = \frac{2V_m}{\pi} \cos(\alpha)$$

$\cos(\alpha)$

$$V_{cont} = \frac{V_i \left[\cos\left(\frac{2\pi t}{T}\right) + 1 \right]}{2} \Rightarrow \cos(\alpha) = \frac{2V_{cont}}{V_i} - 1$$

$$\overline{V_{out}} = \frac{2V_m}{\pi} \left[\frac{2V_{cont}}{V_i} - 1 \right]$$

$$\overline{V_{out}} = K \cos(K, V_{cont})$$

Presenter: Dr. Firuz Zare

www.peeeb.com