



Welcome to PEEEB



Tutorial 7: Isolated DC-DC Converters

Presenter: Dr. Firuz Zare



www.peeeb.com

Q1: Find a conversion ratio of a flyback converter with a real switch $V_s=k_1$ and a real diode. $V_D=k_2$.

Presenter: Dr. Firuz Zare

www.peeeb.com

Flyback Converter

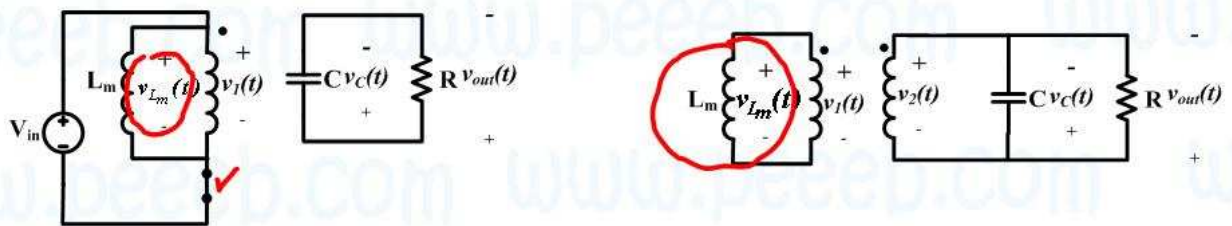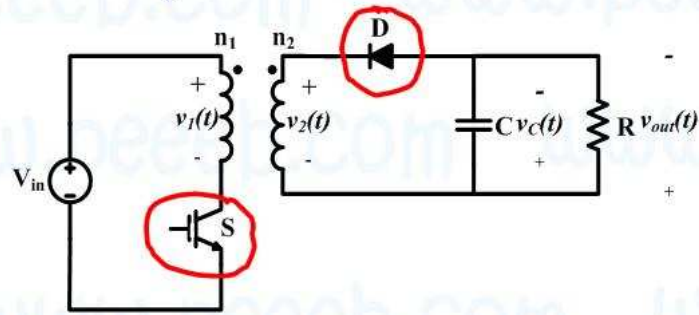


Presenter: Dr. Firuz Zare

www.peeeb.com

$$v_L(t) = V_{in} - V_S \quad \text{on}$$


$$i_C(t) = -i_{out}$$

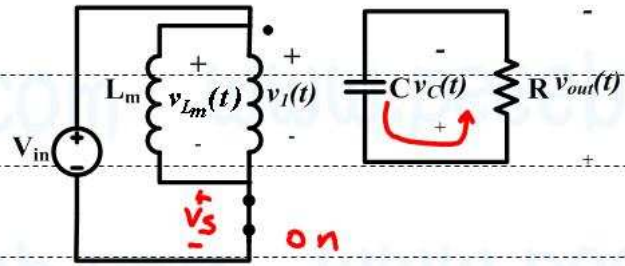

Presenter: Dr. Firuz Zare

www.peeeb.com

$$v_2 = -V_D - v_{out}$$

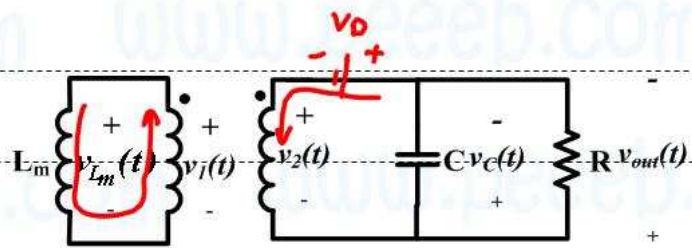

$$\frac{n_1}{n_2} = \frac{v_1}{v_2}$$

$$v_1 = \left(\frac{n_1}{n_2}\right) (-V_D - v_{out})$$

$$v_1 = v_{Lm} = -\left(\frac{n_1}{n_2}\right) (V_D + v_{out}) \quad \overline{v_{Lm}} = 0$$

$$\overline{V_L} = 0$$

$$D T_{sw} (V_{in} - V_S) - D' T_{sw} (V_D + V_{out}) \left(\frac{n_1}{n_2} \right) = 0$$

$$D V_{in} - D V_S - D' V_D \left(\frac{n_1}{n_2} \right) = D' \left(\frac{n_1}{n_2} \right) V_{out} - (V_D + V_{out}) \left(\frac{n_1}{n_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{D}{D' \left(\frac{n_2}{n_1} \right)} - \frac{D V_S}{D' \left(\frac{n_1}{n_2} \right) V_{in}} - \frac{V_D}{V_{in}}$$

$$\frac{V_{out}}{V_{in}} = \frac{D}{D'} \times \left(\frac{n_2}{n_1} \right) - \frac{D}{D'} \times \left(\frac{n_2}{n_1} \right) \left(\frac{V_S}{V_{in}} \right) - \frac{V_D}{V_{in}}$$

Presenter: Dr. Firuz Zare

www.peeeb.com

Q2: In a forward converter, turns ratio N_1/N_2 should be maximum. Find the turns ratios N_1/N_3 and N_1/N_2 .

$$V_{in} = 100 - 140 \text{ V}$$

$$V_{out} = 10 \text{ V}$$

$$N_1/N_2 < 7$$

$$N_3/N_1 > 2$$

$$\frac{V_{out}}{V_{in}} = \frac{N_2}{N_1} \times D$$

$$\frac{10}{100} = \frac{N_2}{N_1} \times D \Rightarrow \frac{N_1}{N_2} = 10 \times D$$

$$\frac{10}{140} = \frac{N_2}{N_1} \times D \Rightarrow \frac{N_1}{N_2} = 14 \times D$$

$$D_{max} = \frac{1}{1 + \frac{N_3}{N_1}} = \frac{1}{1 + 2} = \frac{1}{3} = 0.33$$

Presenter: Dr. Firuz Zare

www.peeeb.com

$$D = 0.33$$

$$\left(\frac{N_1}{N_2}\right) = 10 \times D = 10 \times 0.33 = 3.3 \checkmark ?$$

$$\left(\frac{N_1}{N_2}\right) = 14 \times D = 14 \times 0.33 = 4.62 ?$$

$$\frac{10}{100} = \frac{1}{3.3} \times D \Rightarrow D = 0.33$$

$$\frac{10}{140} = \frac{1}{3.3} \times D \Rightarrow D = 0.237 < 0.33$$

Presenter: Dr. Firuz Zare

www.peeeb.com